


IN THE NAME OF ALLAH, THE MOST GRACIOUS, THE MOST MERCIFUL

# DC Circuits

## 1) Resistors 'R'

Function : resist or limit electrical current in a circuit .

Unit : ohm ' $\Omega$ '

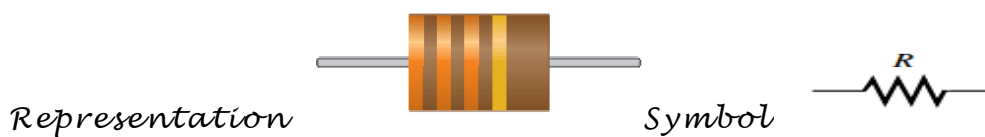


Note : parameters associated with a resistor 1) length ( $l$ ) 2) cross-section area ( $A$ ) .

## 2) Capacitors 'C' OR called condensers

Function : store electrical charge .


Unit : Farad 'F'

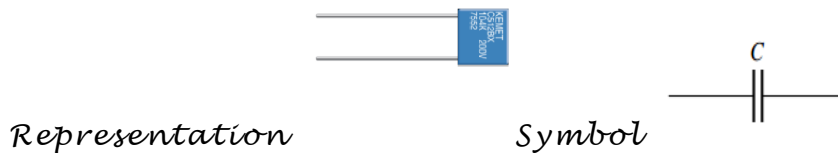

## 3) Inductors 'L' or called coils


Function : used to store energy in an electromagnetic field .

Unit : Henry 'H'

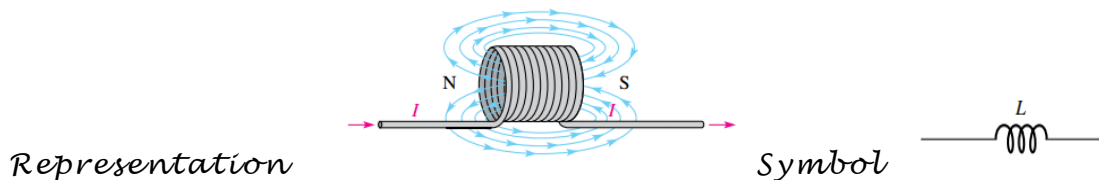
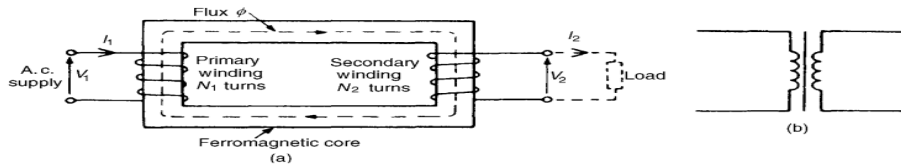
## 4) Transformers

Function : they are used to couple ac voltage from one point in a circuit to another , or to increase or decrease the ac voltage .



## Electronic Devices :

- 1) Voltmeter : measure voltage .
- 2) Ammeter : measure electrical current .
- 3) Ohmmeter : measure resistance .
- 4) Multimeter : measure voltage, electrical current, electrical current .
- 5) Oscilloscope : it is an instrument that measures and observes ac voltage .

**Electrical units :** electrical quantities & their correspond with SI (System International ) symbols .

*Note : time is not an electrical quantity .*

QUANTITY	SYMBOL	SI UNIT	SYMBOL
Capacitance	$C$	Farad	F
Charge	$Q$	Coulomb	C
Conductance	$G$	Siemens	S
Energy (work)	$W$	Joule	J
Frequency	$f$	Hertz	Hz
Impedance	$Z$	Ohm	$\Omega$
Inductance	$L$	Henry	H
Power	$P$	Watt	W
Reactance	$X$	Ohm	$\Omega$
Resistance	$R$	Ohm	$\Omega$
Voltage	$V$	Volt	V

## Powers of ten (Scientific notations ):

Some positive and negative powers of ten.

$10^6 = 1,000,000$	$10^{-6} = 0.000001$
$10^5 = 100,000$	$10^{-5} = 0.00001$
$10^4 = 10,000$	$10^{-4} = 0.0001$
$10^3 = 1,000$	$10^{-3} = 0.001$
$10^2 = 100$	$10^{-2} = 0.01$
$10^1 = 10$	$10^{-1} = 0.1$
$10^0 = 1$	

*Engineering notation* : is a special case of scientific which uses powers of three & its doubles and called metric prefixes ( $10^{\pm 3}$  ,  $10^{\pm 6}$  ,  $10^{\pm 9}$  ,  $10^{\pm 12}$  )

*Metric prefixes* :

METRIC PREFIX	SYMBOL	POWER OF TEN	VALUE
femto	f	$10^{-15}$	one-quadrillionth
pico	p	$10^{-12}$	one-trillionth
nano	n	$10^{-9}$	one-billionth
micro	$\mu$	$10^{-6}$	one-millionth
milli	m	$10^{-3}$	one-thousandth
kilo	k	$10^3$	one thousand
mega	M	$10^6$	one million
giga	G	$10^9$	one billion
tera	T	$10^{12}$	one trillion

----- please take some break :)

*Voltage 'V'* : is expressed as energy divided by charge .

$$V = W/Q$$

*Sources of voltage* :-

- \* *Battery* : converts chemical energy into electrical energy .
- \* *Electronic power supply* : converts ac to dc .
- \* *Solar cell* : converts light into electrical energy .
- \* *Electronic generators* : converts mechanical energy into electrical energy .

*Current* : rate of flow of charges .

$$I = Q/t$$

*Resistance* : is opposition to current .

$$R = V/I$$

### Types of resistors :

#### 1) Fixed resistors :

- a) Carbon resistors
- b) Wire wound resistors

#### 2) Variable resistors :

##### A)

- a) Potentiometer
- b) Rheostat

##### B)

- a) Thermistor
- b) Photoconductive cells

### Resistor color codes :-

First two bands represent value .

Third represents multiplier .

Fourth for tolerance .

band color	Tolerance
Gold	$\pm 5\%$
Silver	$\pm 10\%$
No-band	$\pm 20\%$

Digit	Color
0	black
1	Brown
2	Red
3	Orange
4	yellow
5	green
6	Blue
7	Violet
8	Grey
9	White

Note : if the third band was gold or silver they are calculated as multiplier , where gold = -1 , silver = -2

### Label resistors :-


First three Numbers or Symbols represents value .

Fourth for multiplier.

Fifth for tolerance.

Symbol	F	G	J	K	M	R
Percentage tolerance	$\pm 1\%$	$\pm 2\%$	$\pm 5\%$	$\pm 10\%$	$\pm 20\%$	. (decimal dot)

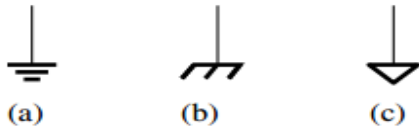**Ground** : is the reference point in electric circuit and has a potential of '0V' wrt other points .



▲ FIGURE 47

Commonly used ground symbols.

Symbol

**Ohm's law**: states the current varies directly with voltage & inversely with resistance .

$$I = V/R$$

**Energy 'W'**: is the fundamental ability to do work .

**Power 'P'**: is the rate at which energy is used .

$$P = W/t$$

**Power rating of resistors 'P<sub>r</sub>'**: it's the max amount of power that resistor can dissipate without being damaged .

**Power dissipate** : is the consumed power .

**Note** : power rating must be greater than power dissipate otherwise the circuit is subjected to resistor failure & resistor is damaged .

**Note** : In problems, if resistor is damaged we consider it short circuit not open circuit .

## Series circuit

**Series circuit** : it's a circuit, which provides only one path for current between 2 given points in a circuit, so the current is the same through each series resistor.

$$I_T = I_1 = I_2 = I_3 = \dots = I_n$$

\* The total resistance of a series circuit is equal to the algebraic sum of resistances of each individual resistor .


$$R_t = R_1 + R_2 + R_3 + \dots + R_n$$

$$R_t = n * R \rightarrow \text{IF } R_1 = R_2 = R_3 = \dots = R_n$$

Ohm's law : -

$$I = V_s / R_t$$

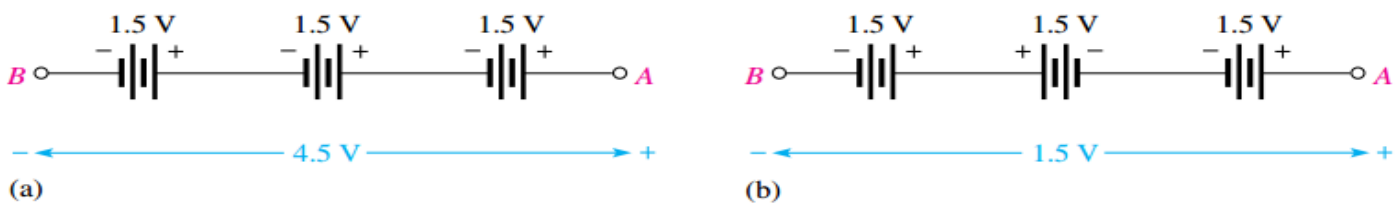**Voltage sources in series :** when 2 or more voltage sources are in series , the total voltage is equal to the algebraic sum of the individual source voltages .



▲ **FIGURE 22**


Voltage sources in series add algebraically. If a source is reversed, it subtracts from the total voltage as shown in part (b). This is not a normal configuration for batteries.

**Kirchhoff's voltage law :** the sum of the voltage drops equals the total voltage source .

$$V_s = V_1 + V_2 + V_3 + \dots + V_n$$

**Voltage divider :**

$$V_x = (R_x / R_t) * V_s$$

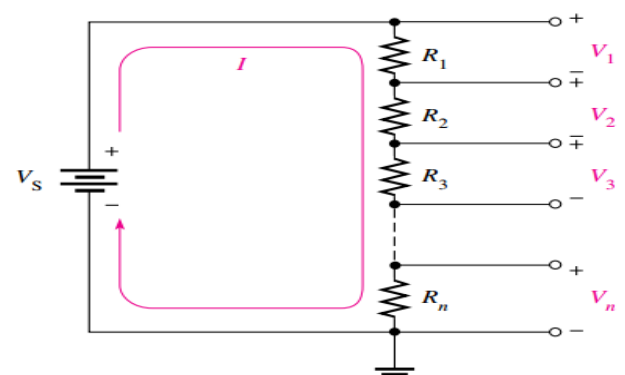

**Power in a series circuit :** the total amount of power in a series resistive circuit is equal to the sum of the powers in each resistor in series .

$$P_t = P_1 + P_2 + P_3 + \dots + P_n$$

where  $P_x = IV_x = i^2 R_x = (V_s)^2 / R_x$

OR  $P_t = IV_s = I^2 R_t = (V_s)^2 / R_t$

## Parallel circuit

**Parallel circuit :** it's a parallel circuit has more than one current path(branches) between 2 given points .

**Voltage drop in parallel circuits :** the voltage across any given branch of a parallel circuit is equal to the voltage drop across each of the other branches in parallel .


$$V_s = V_1 = V_2 = V_3 = \dots = V_n$$

**Kirchhoff current law :** the sum of the currents into a junction ' $I_{T'in'}$ ' is equal to the sum of the currents out of that junction ' $I_{T'out'}$ ' .

$$I_T = I_1 + I_2 + I_3 + \dots + I_n$$

$$I_{T'in'} = I_{T'out'}$$
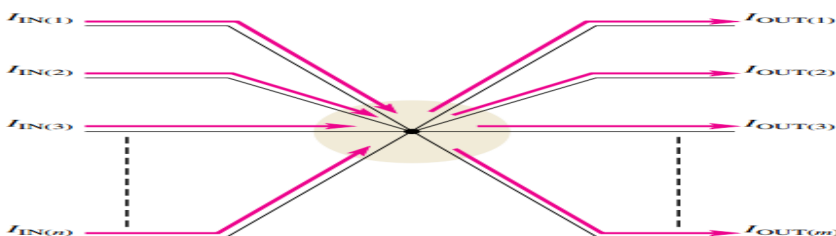
$$I_{1'in'} + I_{2'in'} + I_{3'in'} + \dots + I_{n'in'} = I_{1'out'} + I_{2'out'} + I_{3'out'} + \dots + I_{n'out'}$$



please take some break :)  
it's the last part .

Total parallel resistance :-

$$I_T = I_1 + I_2 + I_3 + \dots + I_n$$

$$\frac{V_S}{R_t} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n}$$

$$\text{But } V_S = V_1 = V_2 = V_3 = \dots = V_n$$

Then

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Then

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}}$$

Special Cases

$$R_T = R/n \rightarrow \text{IF } R_1 = R_2 = R_3 = \dots = R_n$$

$$R_T = \frac{R_1 * R_2}{R_1 + R_2} \rightarrow \text{IF } R_1 \neq R_2, \text{ TWO RESISTORS ONLY}$$

Ohm's law :-

$$I = V_S / R_t$$

Current divider :-



$$I_X = \left( \frac{R_T}{R_X} \right) \times I_T$$

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) \times I_T$$

$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) \times I_T$$

**\*\* ف البسط المقاومة البعيدة ع مجموع المقاومتين , لو اكثر من مقاومتين باحيب المقاومة المكافئة لكل عدا المقاومة اللي عاوز احسب التيار فيها (اشيل المقاومة 2 و احط مكانها المقاومة المكافئة)**


*Power in parallel circuits :-*

$$P_t = P_1 + P_2 + P_3 + \dots + P_n$$

Where  $P_x = IV_x = I^2 R_x = (V_s)^2 / R_x$

OR  $P_t = IV_s = I^2 R_t = (V_s)^2 / R$


## SERIES-PARALLEL CIRCUITS

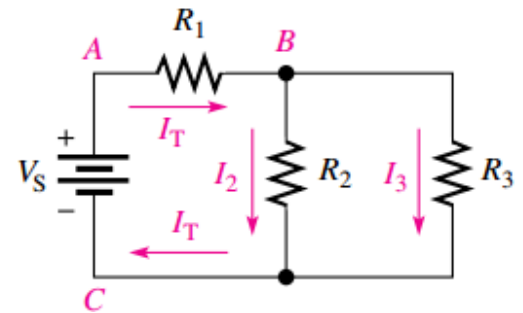

*Series parallel circuits :* A circuit consists of combinations of both series & parallel current paths .

$$R_{2.3} = \frac{R_3 * R_2}{R_3 + R_2} \quad ; \quad R_T = R_1 + R_{2.3}$$

# Capacitors

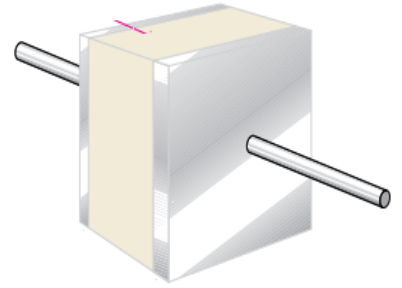

## Capacitance

$$C = Q/V$$

The formula for the energy stored by a capacitor :

$$W = \frac{1}{2}CV^2 = \frac{1}{2}Q^2/C = \frac{1}{2}QV$$

## Series capacitor :-


While charging ,  $I = Q/t$  is the same in circuits , so

both capacitors store the same

amount of charge

$$V_S = V_1 + V_2$$

$$V_S = QT/CT$$

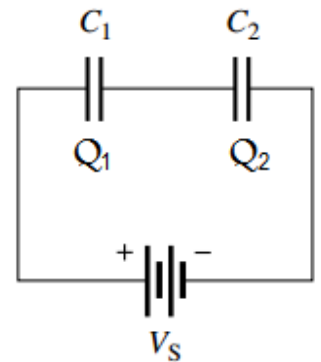

By applying KVL ----->

$$QT/CT = Q1/C1 + Q2/C2$$

## Parallel capacitors :-

the amount of charge on each capacitor is directly proportional to its capacitance value .


$$C = Q/V$$

$$QT = Q1 + Q2$$

$$CT = C1V1 + C2V2$$

$$\text{But } V_S = V1 = V2$$

$$\text{Then } CT = C1 + C2$$

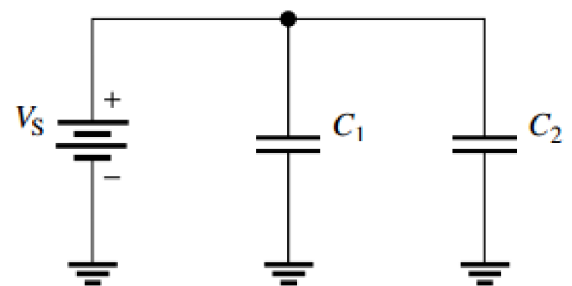

## Series-parallel capacitors :-


- 1) Consider parallel capacitors as series resistances .
- 2) Consider series capacitors as parallel resistances .

## INDUCTORS

Series Inductors : the total inductance is the sum of individual inductances .

$$L_T = L_1 + L_2 + L_3 + \dots + L_n$$


Parallel inductor :
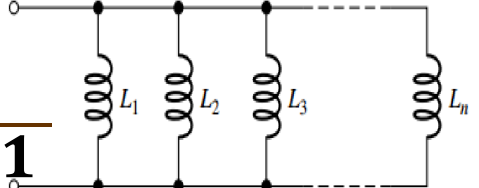
$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}}$$


Important notes :

1- يجب ان تكتب القوانين لحساب كل شيء داخل المسألة

2- ان تكتب الوحدات بعد كل ناتج

3- ان تختار اسهل الطرق لحل المسألة الا اذا طلب الحل بطريقة معينة

4- ف النواتج لا يجب ان تكتب ف صورة كسر اعتيادي و لكن كسر عشري

5- عند كتابة ناتج به كسر عشري يكتب العلامة العشرية (.) و ليس (,)

6- ال(,) تستخدم ف الناتج بعد كل 3 ارقام داخل العدد و لايفضل استخدامها ف الامتحان لعدم التشبث

7- ف مسائل السيريس باراليل يفضل تحويل الدائرة الي ابسط ما يمكن ثم حساب المطلوب مع التوضيح بالرسم خلال كل خطوة من التبسيط

## 9- PART OF NETWORK THEOREMS IN ANOTHER PDF

\*WILL BE MADE & UPLOADED SOON\*

8- والله لازم تكتب القوانين ☺

10- حل الشيتات مهم لان الدكتور عاوز يعرف انت بتذاكر و المحتوي وصلك ولا لا هو مش بيعملك اختبار ذكاء .

\* pictures from floyd

# تم بحمد الله

made by  
**TOM**

please read it again , carefully & well-understanding ^-^